

ECE 645: Lecture 5

Fast Adders:

**Parallel Prefix Network Adders,
Conditional-Sum Adders,
& Carry-Skip Adders**

Required Reading

Behrooz Parhami,

Computer Arithmetic: Algorithms and Hardware Design

Chapter 6.4, Carry Determination as Prefix Computation

Chapter 6.5, Alternative Parallel Prefix Networks

Chapter 7.4, Conditional-Sum Adder

Chapter 7.5, Hybrid Adder Designs

Chapter 7.1, Simple Carry-Skip Adders

Note errata at:

http://www.ece.ucsb.edu/~parhami/text_comp_arit_1ed.htm#errors

Recommended Reading

*J-P. Deschamps, G. Bioul, G. Sutter,
Synthesis of Arithmetic Circuits: FPGA, ASIC and
Embedded Systems*

Chapter 11.1.9, Prefix Adders

Chapter 11.1.3, Carry-Skip Adder

Chapter 11.1.4, Optimization of Carry-Skip Adders


Chapter 11.1.10, FPGA Implementations of Adders

Chapter 11.1.11, Long-Operand Adders

Parallel Prefix Network Adders

Parallel Prefix Network Adders

Basic component - Carry operator (1)

 


$$g = g'' + g'p''$$

$$p = p'p''$$

$$(g, p) = (g', p') \circ (g'', p'') = (g'' + g'p'', p'p'')$$

Parallel Prefix Network Adders

Basic component - Carry operator (2)

 

$$g = g'' + g'p''$$
$$p = p'p''$$

$$(g, p) = (g', p') \circ (g'', p'') = (g'' + g'p'', p'p'')$$

Properties of the carry operator $\dot{\smash{\circ}}$

Associative

$$[(g_1, p_1) \dot{\smash{\circ}} (g_2, p_2)] \dot{\smash{\circ}} (g_3, p_3) = (g_1, p_1) \dot{\smash{\circ}} [(g_2, p_2) \dot{\smash{\circ}} (g_3, p_3)]$$

Not commutative

$$(g_1, p_1) \dot{\smash{\circ}} (g_2, p_2) \neq (g_2, p_2) \dot{\smash{\circ}} (g_1, p_1)$$

Parallel Prefix Network Adders

Major concept

Given:

$$(g_0, p_0) \quad (g_1, p_1) \quad (g_2, p_2) \quad \dots \quad (g_{k-1}, p_{k-1})$$

Find:

$$(g_{[0,0]}, p_{[0,0]}) \quad (g_{[0,1]}, p_{[0,1]}) \quad (g_{[0,2]}, p_{[0,2]}) \quad \dots \quad (g_{[0,k-1]}, p_{[0,k-1]})$$

$$c_i = g_{[0,i-1]} + c_0 p_{[0,i-1]}$$

↖
block generate
from index 0
to k-1

Similar to Parallel Prefix Sum Problem

Parallel Prefix Sum Problem

Given:

$$x_0 \quad x_1 \quad x_2 \quad \dots \quad x_{k-1}$$

Find:

$$x_0 \quad x_0 + x_1 \quad x_0 + x_1 + x_2 \quad \dots \quad x_0 + x_1 + x_2 + \dots + x_{k-1}$$

Parallel Prefix Adder Problem

Given:


$$x_0 \quad x_1 \quad x_2 \quad \dots \quad x_{k-1}$$

Find:

$$x_0 \quad x_0 \text{ } \not\subset \text{ } x_1 \quad x_0 \text{ } \not\subset \text{ } x_1 \text{ } \not\subset \text{ } x_2 \quad \dots \quad x_0 \text{ } \not\subset \text{ } x_1 \text{ } \not\subset \text{ } x_2 \text{ } \not\subset \text{ } \dots \text{ } \not\subset \text{ } x_{k-1}$$

where $x_i = (g_i, p_i)$

Parallel Prefix Sums Network I

 

Parallel Prefix Sums Network I – Cost (Area) Analysis

$$\begin{aligned}\text{Cost} = C(k) &= 2 C(k/2) + k/2 = \\ &= 2 [2C(k/4) + k/4] + k/2 = 4 C(k/4) + k/2 + k/2 = \\ &= \dots = \\ &= 2^{\log_2 k - 1} C(2) + k/2 (\log_2 k - 1) = \\ &= k/2 \log_2 k\end{aligned}$$

$$C(2) = 1$$

Example:

$$\begin{aligned}C(16) &= 2 C(8) + 8 = 2[2 C(4) + 4] + 8 = \\ &= 4 C(4) + 16 = 4 [2 C(2) + 2] + 16 = \\ &= 8 C(2) + 24 = 8 + 24 = \mathbf{32} = (16/2) \log_2 16\end{aligned}$$


Parallel Prefix Sums Network I – Delay Analysis

$$\begin{aligned}\text{Delay} = \mathbf{D(k)} &= D(k/2) + 1 = \\ &= [D(k/4) + 1] + 1 = D(k/4) + 1 + 1 = \\ &= \dots = \\ &= \log_2 k\end{aligned}\quad \left| \begin{array}{l} D(2) = 1 \end{array} \right|$$

 Example:

$$\begin{aligned}\mathbf{D(16)} &= D(8) + 1 = [D(4) + 1] + 1 = \\ &= D(4) + 2 = [D(2) + 1] + 2 = \\ &= 4 = \log_2 16\end{aligned}$$

Parallel Prefix Sums Network II (Brent-Kung)



Parallel Prefix Sums Network II – Cost (Area) Analysis

$$\begin{aligned}\text{Cost} = C(k) &= C(k/2) + k - 1 = \\ &= [C(k/4) + k/2 - 1] + k - 1 = C(k/4) + 3k/2 - 2 = \\ &= \dots = \\ &= C(2) + (2k - 2k/2^{\log_2 k - 1}) - (\log_2 k - 1) = \\ &= 2k - 2 - \log_2 k\end{aligned}\quad \left| \begin{array}{l} C(2) = 1 \end{array} \right|$$

Example:

$$\begin{aligned}C(16) &= C(8) + 16 - 1 = [C(4) + 8 - 1] + 16 - 1 = \\ &= C(2) + 4 - 1 + 24 - 2 = 1 + 28 - 3 = \mathbf{26} \\ &= 2 \cdot 16 - 2 - \log_2 16\end{aligned}$$

Parallel Prefix Sums Network II – Delay Analysis


$$\begin{aligned}\text{Delay} = \mathbf{D(k)} &= D(k/2) + 2 = \\ &= [D(k/4) + 2] + 2 = D(k/4) + 2 + 2 = \\ &= \dots = \\ &= \mathbf{2 \log_2 k - 1}\end{aligned}\quad \left| \begin{array}{l} D(2) = 1 \end{array} \right|$$

Example:

$$\begin{aligned}\mathbf{D(16)} &= D(8) + 2 = [D(4) + 2] + 2 = \\ &= D(4) + 4 = [D(2) + 2] + 4 = \\ &= \mathbf{7} = 2 \log_2 16 - 1\end{aligned}$$

8-bit Brent-Kung Parallel Prefix Network

4-bit Brent-Kung Parallel Prefix Network

 

8-bit Brent-Kung Parallel Prefix Network Critical Path

Critical Path

GP

$$g_i = x_i \cdot y_i$$

$$p_i = x_i \oplus y_i$$

1 gate delay

ϕ

$$g = g'' + g' p''$$

$$p = p' p''$$

2 gate delays

C

$$c_{i+1} = g_{[0,i]} + c_0 p_{[0,i]}$$


2 gate delays

S


$$s_i = p_i \oplus c_i$$

1 gate delay

 Brent-Kung Parallel Prefix Graph for 16 Inputs



 Kogge-Stone Parallel Prefix Graph for 16 Inputs




Parallel Prefix Network Adders


Comparison of architectures

	Network 2 Brent-Kung	Hybrid	Kogge-Stone
Delay(k)	$2 \log_2 k - 2$	$\log_2 k + 1$	$\log_2 k$
Cost(k)	$2k - 2 - \log_2 k$	$k/2 \log_2 k$	$k \log_2 k - k + 1$
Delay(16)	6	5	4
Cost(16)	26	32	49
Delay(32)	8	6	5
Cost(32)	57	80	129

Latency vs. Area Tradeoff

 


B-K: Six levels, 26 cells

 

K-S: Four levels, 49 cells


Hybrid Brent-Kung/Kogge-Stone Parallel Prefix Graph for 16 Inputs

Hybrid: Five levels, 32 cells

 


Conditional-Sum Adders

One-level k-bit Carry-Select Adder

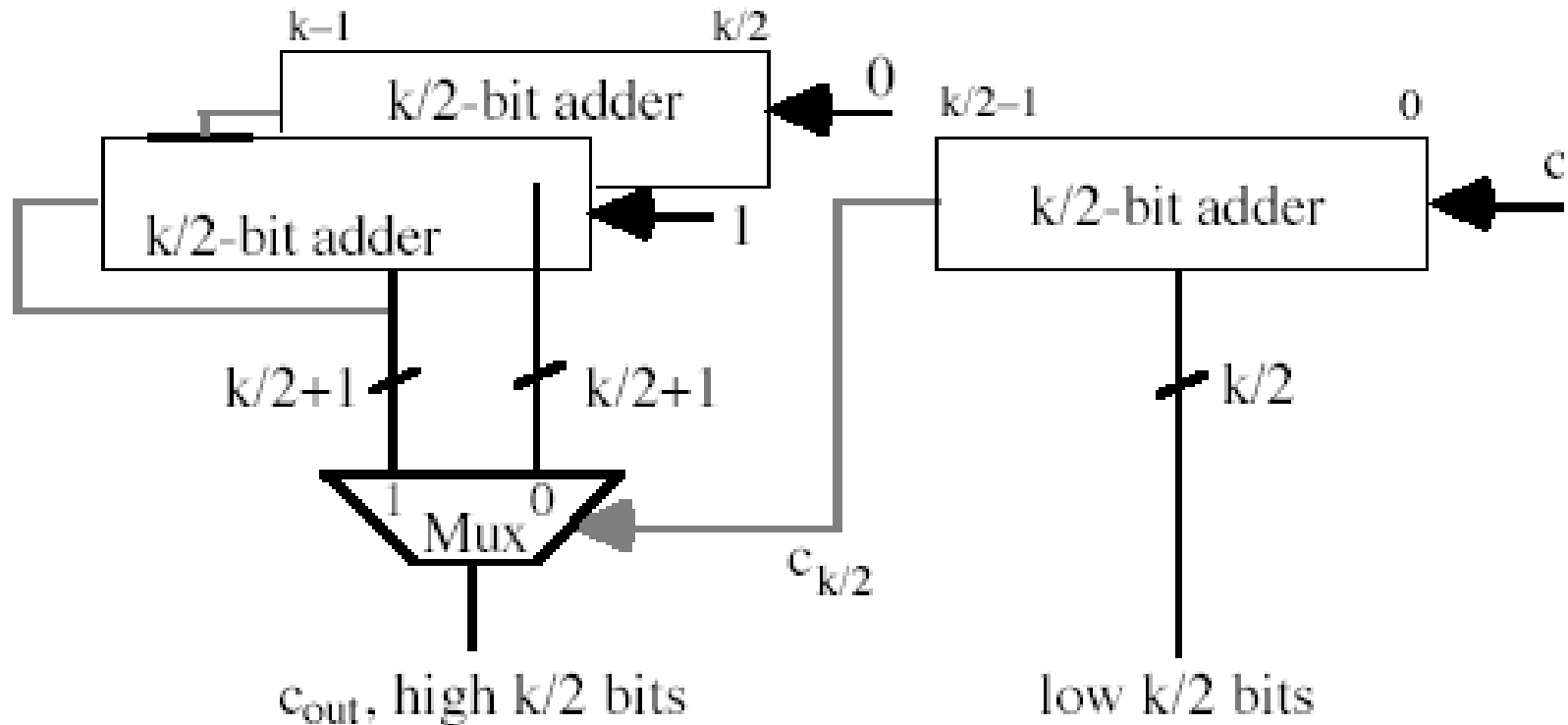

Two-level k-bit Carry Select Adder

 

Conditional Sum Adder

Extension of carry-select adder

Carry select adder

- One-level using $k/2$ -bit adders

- Two-level using $k/4$ -bit adders


- Three-level using $k/8$ -bit adders

- Etc.


Assuming k is a power of two, eventually have an extreme where there are $\log_2 k$ -levels using 1-bit adders

- This is a conditional sum adder

 Conditional Sum Adder. Top-Level Block for One Bit Position



Three Levels of a Conditional Sum Adder

 

• branch point
• concatenation

$1+1$

$2+1$

$4+1$

block carry-in
determines selection

16-Bit Conditional Sum Adder Example

Block width	Block carry-in		x	0	0	1	0	0	1	1	0	1	1	1	0	1	0	1	0	
			y	0	1	0	0	1	0	1	1	0	1	0	1	1	1	0	1	0
			Block sum and block carry-out																	C _{in}
			15 14 13 12 11 10 9 8 7 6 5 4 3 2 1 0																	
1	0	s	0	1	1	0	1	1	0	1	1	0	1	1	0	1	1	0	1	
	c	0	0	0	0	0	0	0	1	0	0	0	1	0	0	1	0	0	0	
1	1	s	1	0	0	1	0	0	1	0	0	1	0	0	1	0	0	0		
	c	0	1	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1		
2	0	s	0	1	1	0	1	1	0	1	0	0	1	1	0	1	1	1		
	c	0		0		0		1		1		1		0		1		0		
1	1	s	1	0	1	1	0	0	1	0	0	1	0	0	1	0				
	c	0		0		1		1		1		1		1		1				
4	0	s	0	1	1	0	0	0	0	1	0	0	1	1	0	1	1	1		
	c	0				1					1				1					
1	1	s	0	1	1	1	0	0	1	0	0	1	0	0						
	c	0				1					1									
8	0	s	0	1	1	1	0	0	0	1	0	1	0	0	0	1	1	1		
	c	0								1	1									
1	1	s	0	1	1	1	0	0	1	0										
	c	0							1	0										
16	0	s	0	1	1	1	0	0	1	0	0	1	0	0	0	1	1	1		
	c	0																		
1	1	s																		
	c																			

C_{out}

C_{out}

Conditional Sum Adder Metrics

Multilevel carry-select idea carried out to the extreme, until we arrive at single-bit blocks.

$$C(k) \approx 2C(k/2) + k + 2 \approx k (\log_2 k + 2) + k C(1)$$


$$T(k) = T(k/2) + 1 = \log_2 k + T(1)$$

where $C(1)$ and $T(1)$ are the cost and delay of the circuit of Fig. 7.11 used at the top to derive the sum and carry bits with a carry-in of 0 and 1


The term $k + 2$ in the first recurrence represents an upper bound on the number of single-bit 2-to-1 multiplexers needed for combining two $k/2$ -bit adders into a k -bit adder

Hybrid Adders

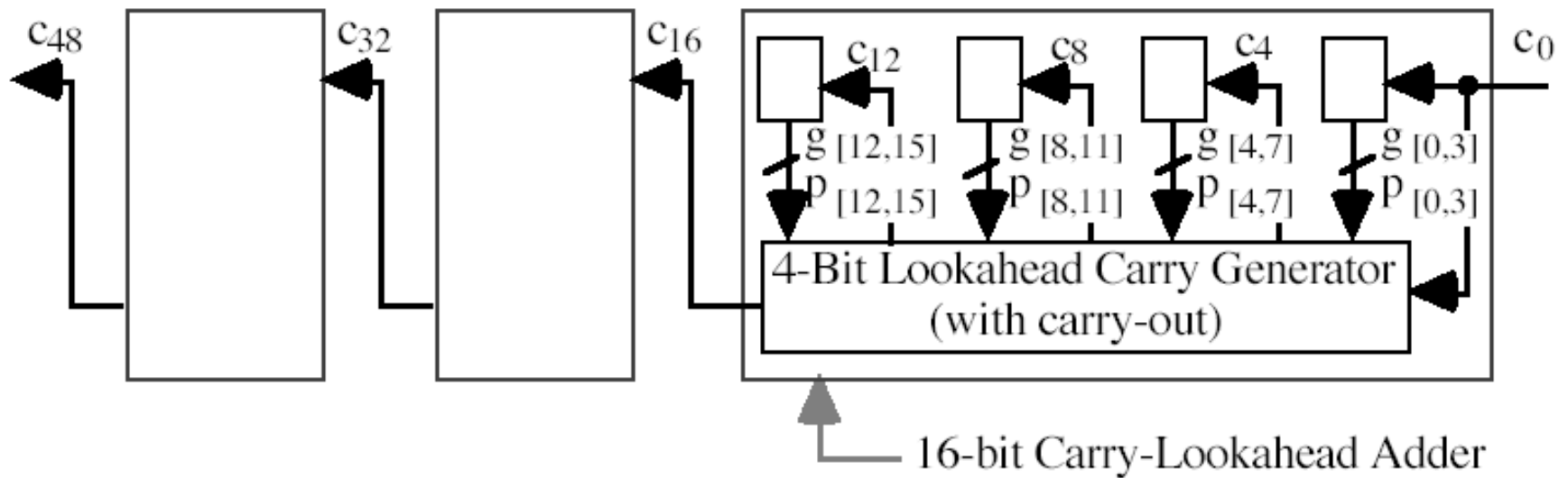A Hybrid Ripple-Carry/Carry-Lookahead Adder



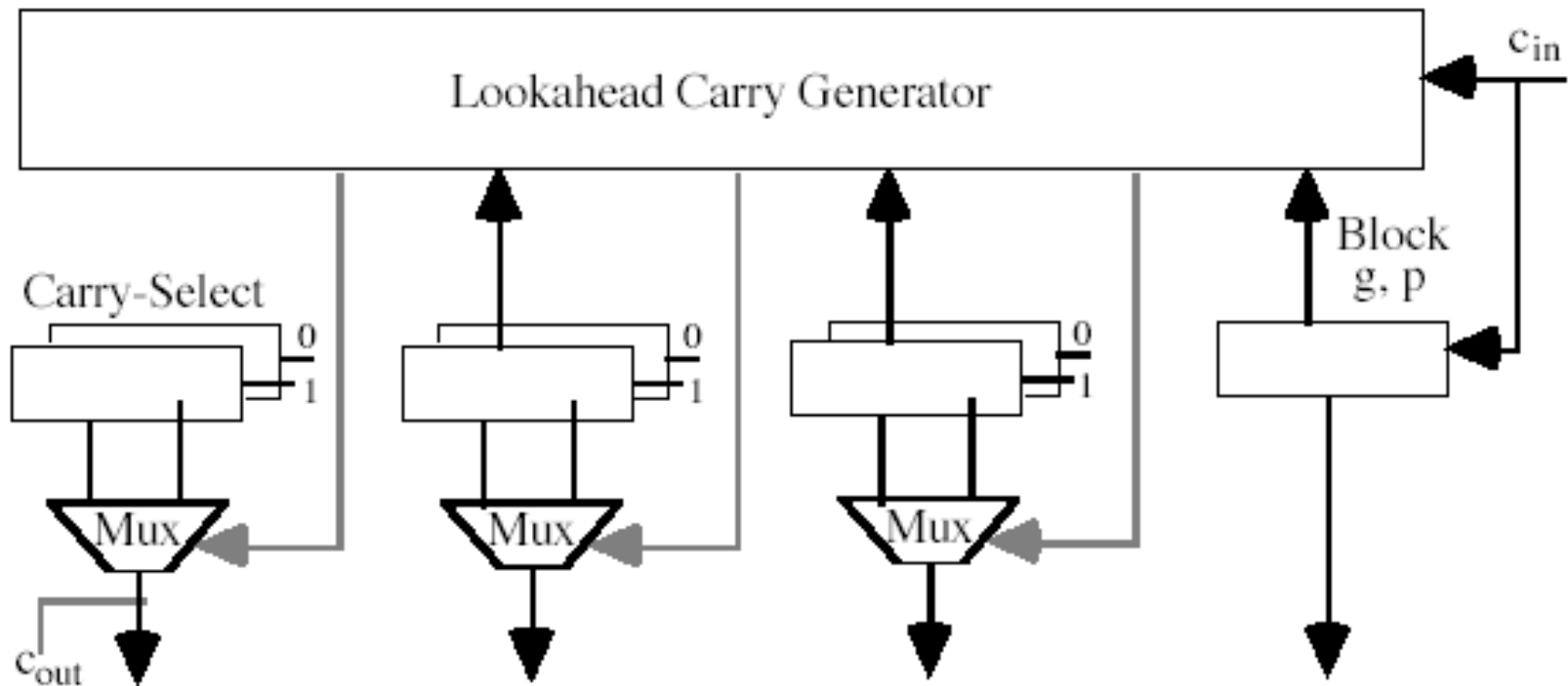A Hybrid Carry-Lookahead/Carry-Select Adder



Carry-Skip Adders

Fixed-Block-Size

7.1 Simple Carry-Skip Adders


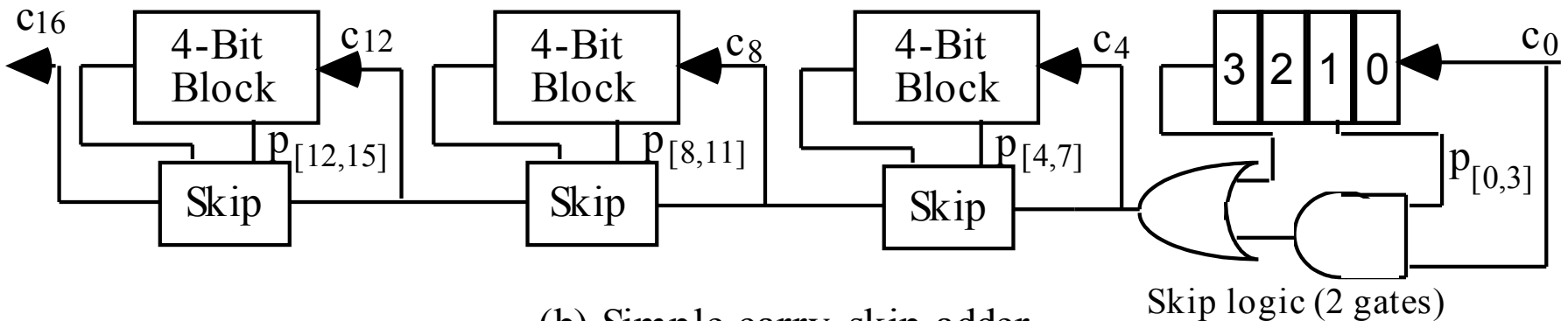
 


Fig. 7.1 Converting a 16-bit ripple-carry adder into a simple carry-skip adder with 4-bit skip blocks.


Another View of Carry-Skip Addition

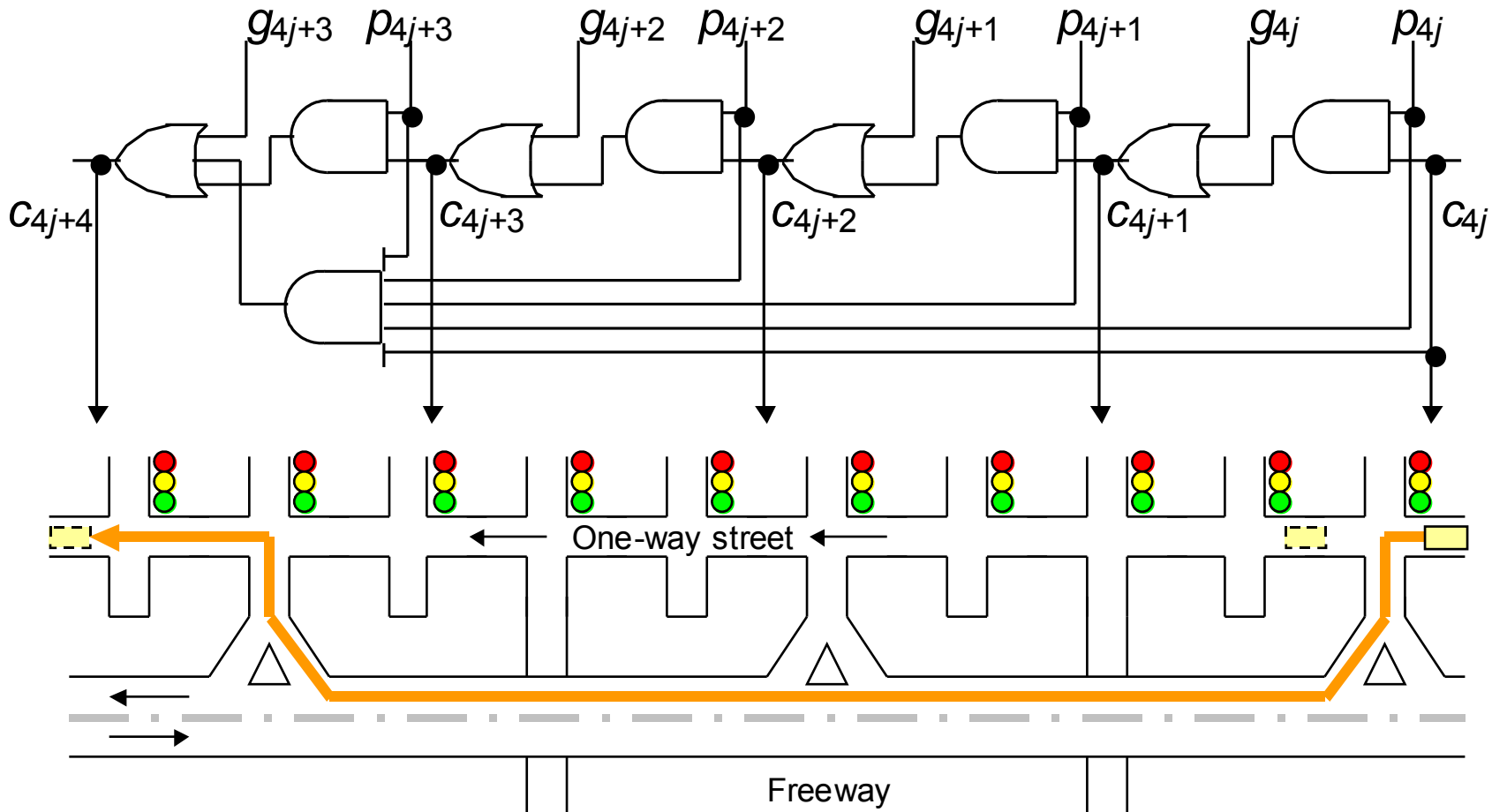

Street/freeway analogy for carry-skip adder.

Mux-Based Skip Carry Logic

Fig. 10.7 of arch book

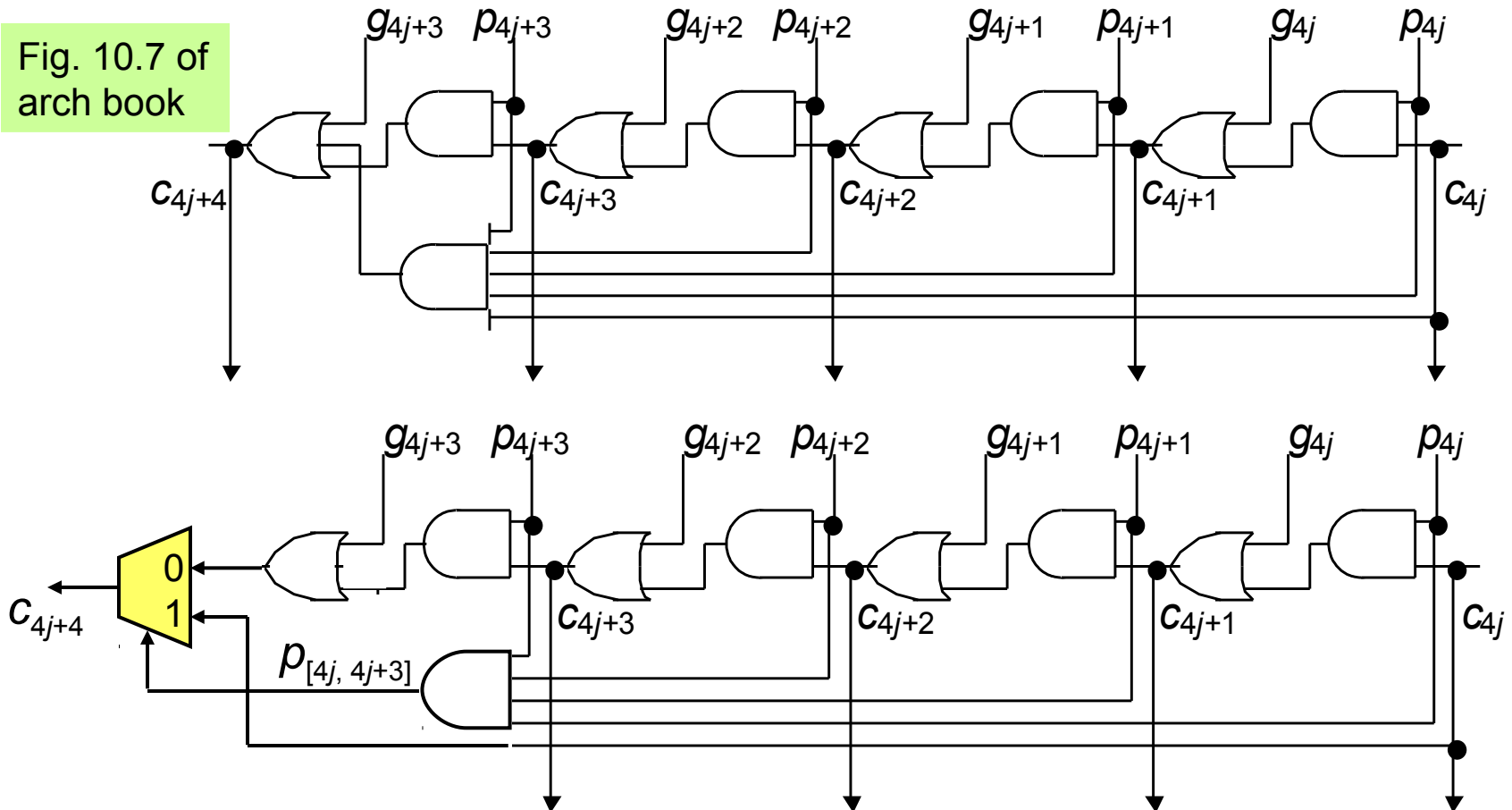

The carry-skip adder with “OR combining” works fine if we begin with a clean slate, where all signals are 0s at the outset; otherwise, it will run into problems, which do not exist in mux-based version

Carry-Skip Adder with Fixed Block Size


Block width b ; k/b blocks to form a k -bit adder (assume b divides k)

$$T_{\text{fixed-skip-add}} = \underbrace{(b-1)}_{\text{in block 0}} + \underbrace{0.5}_{\text{OR gate}} + \underbrace{(k/b - 2)^1}_{\text{skips}} + \underbrace{(b-1)}_{\text{in last block}}$$

$$\cong 2b + k/b - 3.5 \text{ stages}$$

$$dT/db = 2 - k/b^2 = 0 \quad \Rightarrow \quad b^{\text{opt}} = \sqrt{k/2}$$

$$T^{\text{opt}} = 2\sqrt{2k} - 3.5$$

 

Example: $k = 32$, $b^{\text{opt}} = 4$, $T^{\text{opt}} = 12.5$ stages
(contrast with 32 stages for a ripple-carry adder)

Fixed-Block-Size Carry-Skip Adder (1)

Notation & Assumptions

Adder size - k-bits

Fixed block size - b bits

Number of stages - t

Delay of skip logic = Delay of one stage of ripple-carry adder
= 1 delay unit


Latency of the carry-skip adder with fixed block width

$$\begin{aligned} \text{Latency}_{\text{fixed-carry-skip}} &= \underbrace{(b - 1)}_{\text{in block 0}} + \underbrace{0.5}_{\text{OR gate}} + \underbrace{\frac{k}{b} - 2}_{\text{skips}} + \underbrace{(b - 1)}_{\text{in last block}} \\ &= 2b + \frac{k}{b} - 3.5 \end{aligned}$$

Fixed-Block-Size Carry-Skip Adder (2)

Optimal fixed block size
 
$$\frac{d\text{Latency}_{\text{fixed-carry-skip}}}{db} = 2 - \frac{k}{b^2} = 0$$



$$b_{\text{opt}} = \sqrt{\frac{k}{2}} \quad t_{\text{opt}} = \left\lceil \frac{k}{b_{\text{opt}}} \right\rceil = \sqrt{2k}$$

$$\text{Latency}_{\text{fixed-carry-skip}}^{\text{opt}} = 2 \sqrt{\frac{k}{2}} + \frac{k}{\sqrt{\frac{k}{2}}} - 3.5 =$$

$$= \sqrt{2k} + \sqrt{2k} - 3.5 = \boxed{2\sqrt{2k} - 3.5}$$


Fixed-Block-Size Carry-Skip Adder (3)

k	b _{opt}	t _{opt}	Latency _{fixed-carry-skip}	Latency _{ripple-carry}	Latency _{look-ahead}
32	4	8	12.5	32	6.5
128	8	16	28.5	128	8.5
16	2	8	8.5	16	4.5
	3	5	7.5		
64	5	13	18.5	64	6.5
	6	11	18.5		


Carry-Chain & Carry-Skip Adders in Xilinx FPGAs

Basic Cell of a Carry-Chain Adder in Xilinx FPGAs


x_i	y_i	c_{i+1}
0	0	y_i
0	1	c_i
1	0	c_i
1	1	y_i

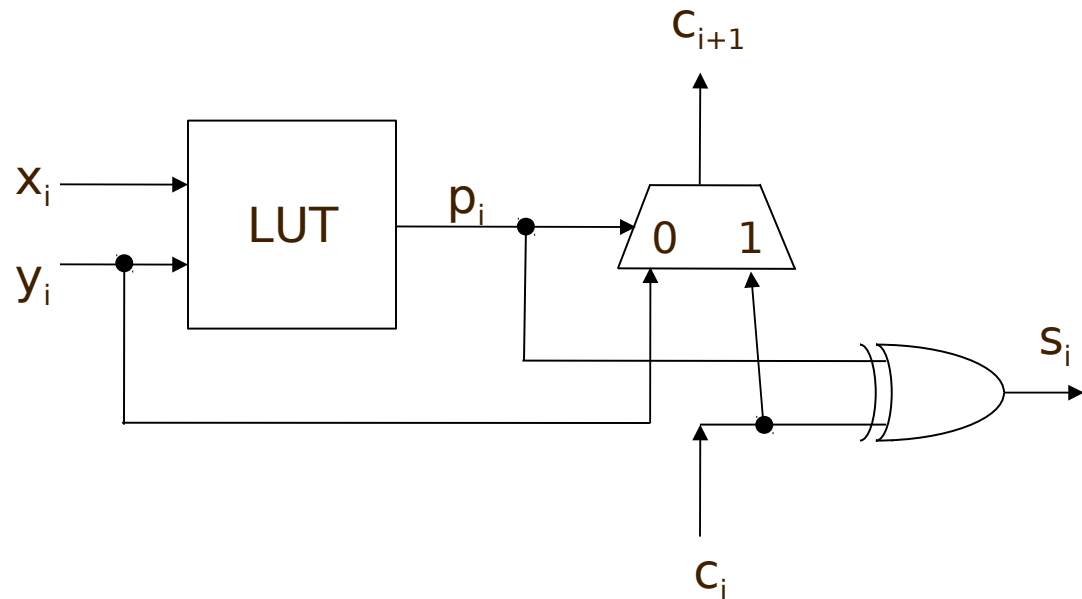


Carry-Skip Adder b-bit block

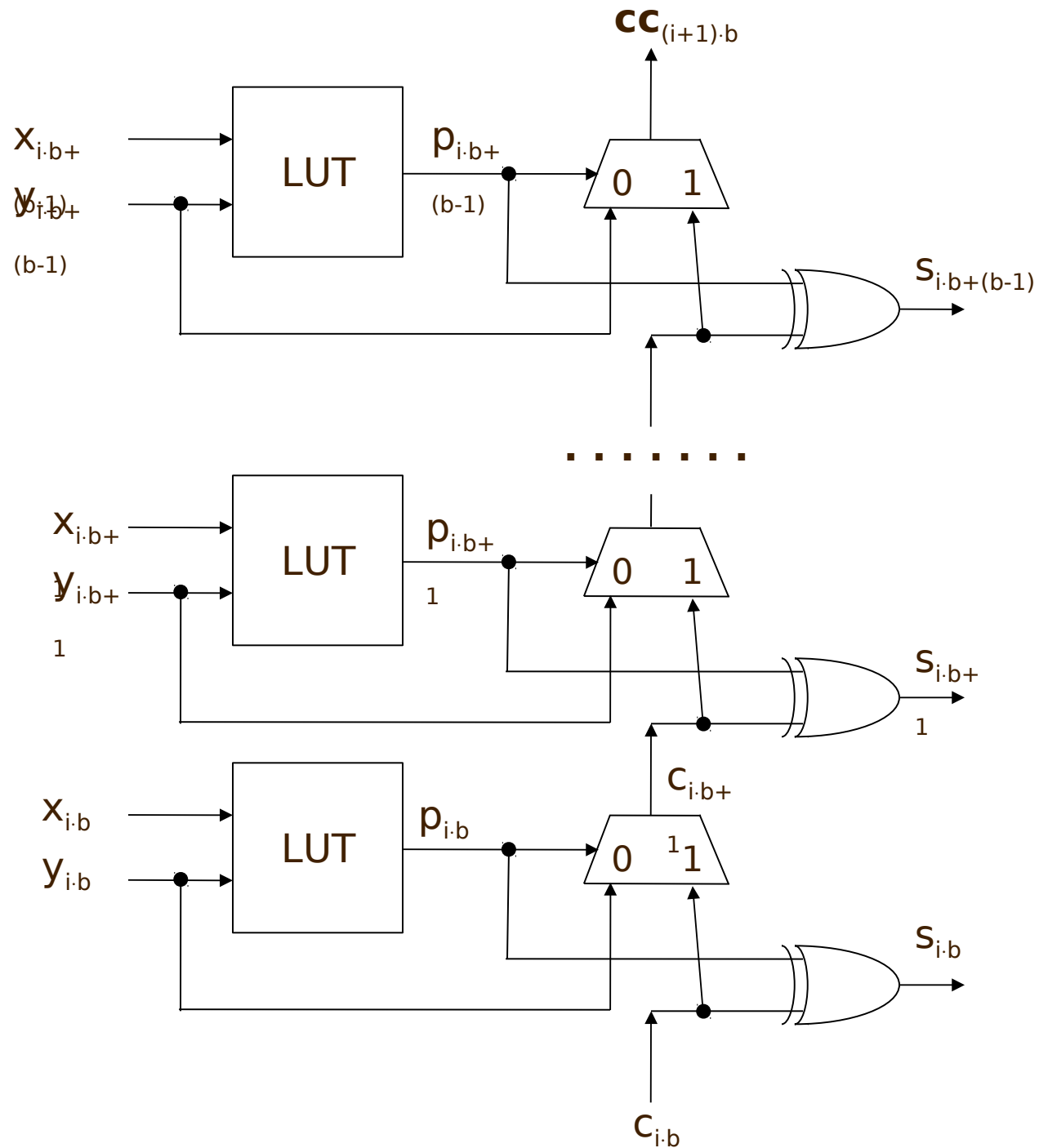

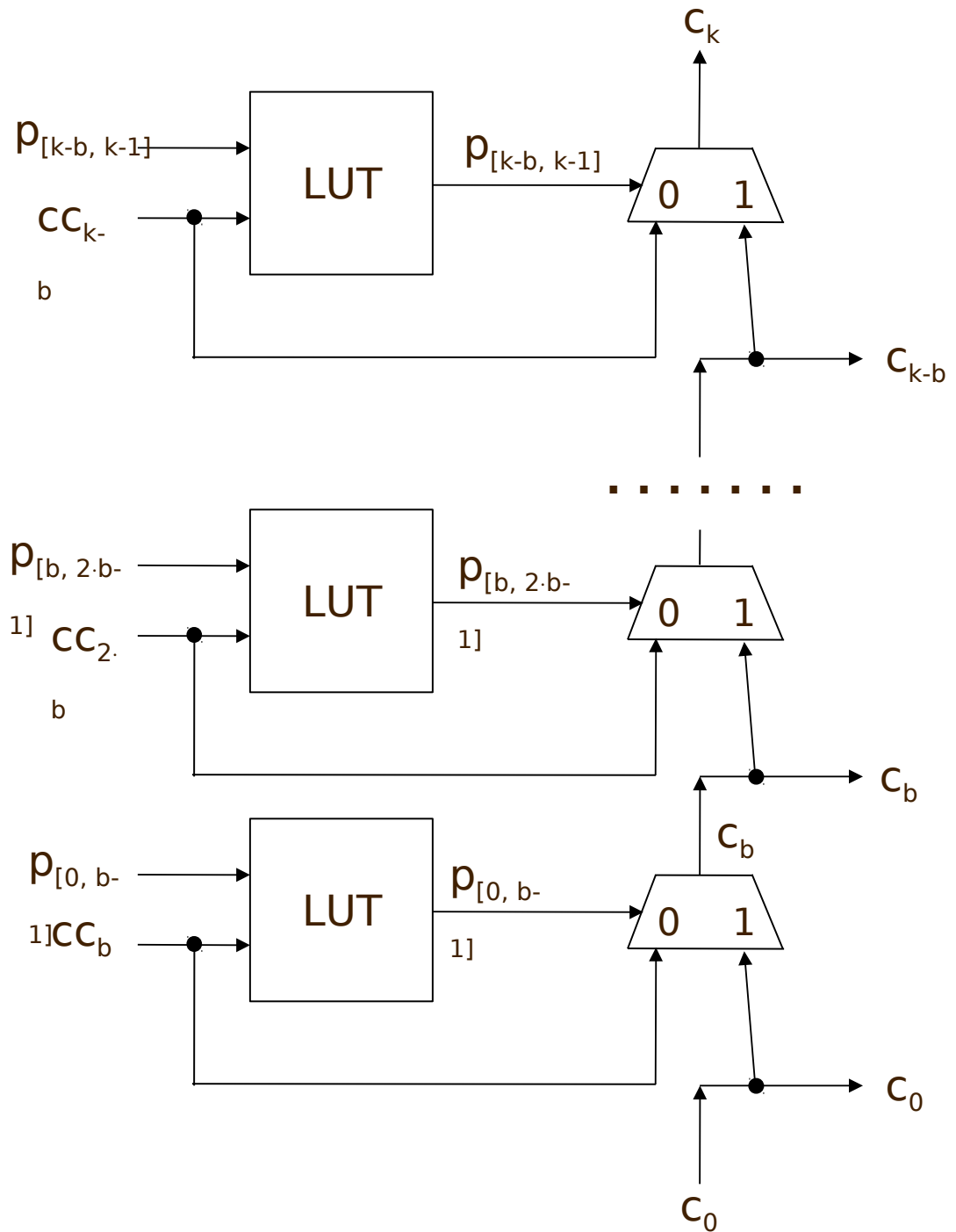
Carry-Skip Adder: Carry Skip Multiplexers



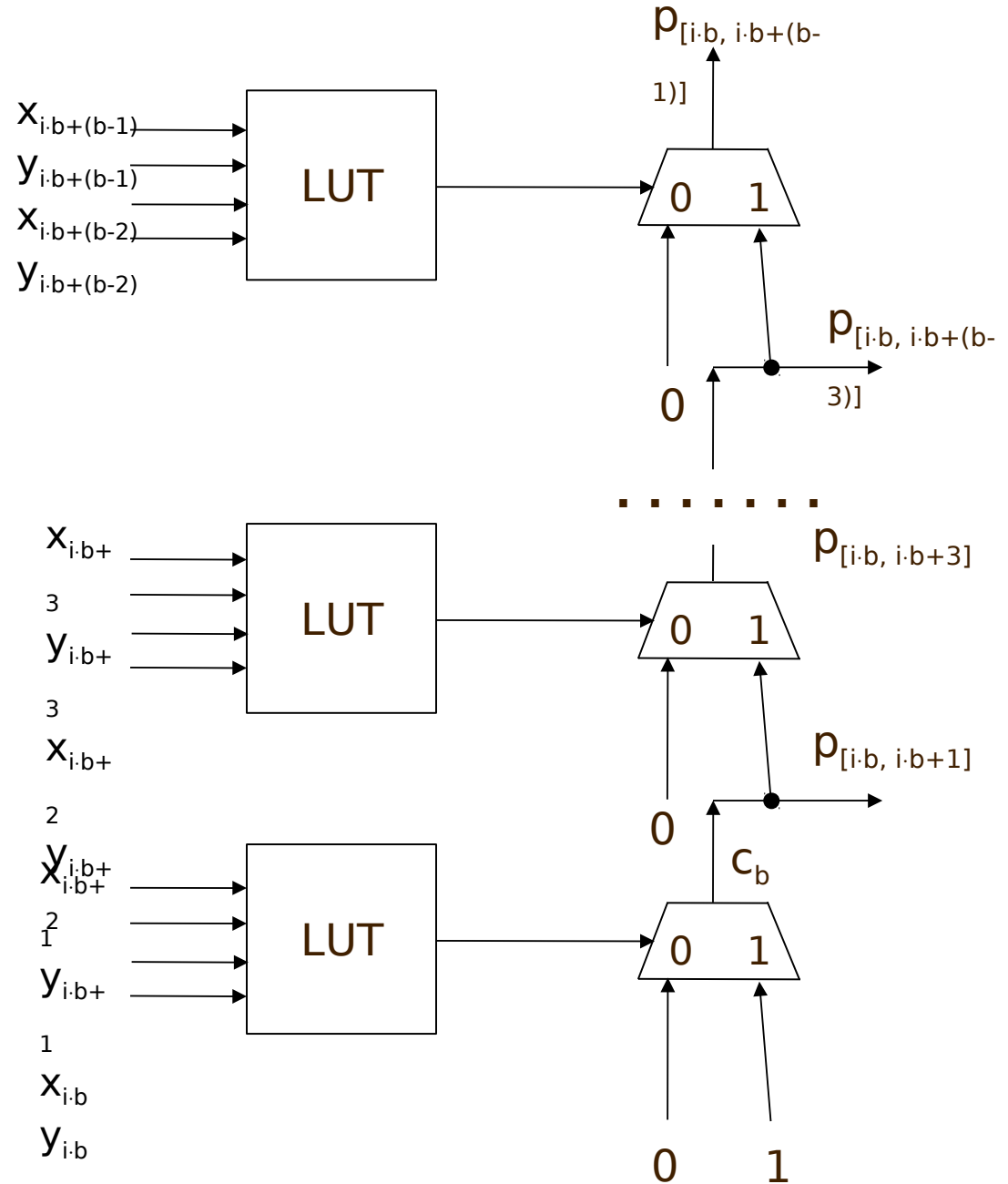Carry-Skip Adder: Computation of the Block Propagate Signals



Complete Carry-Skip Adder

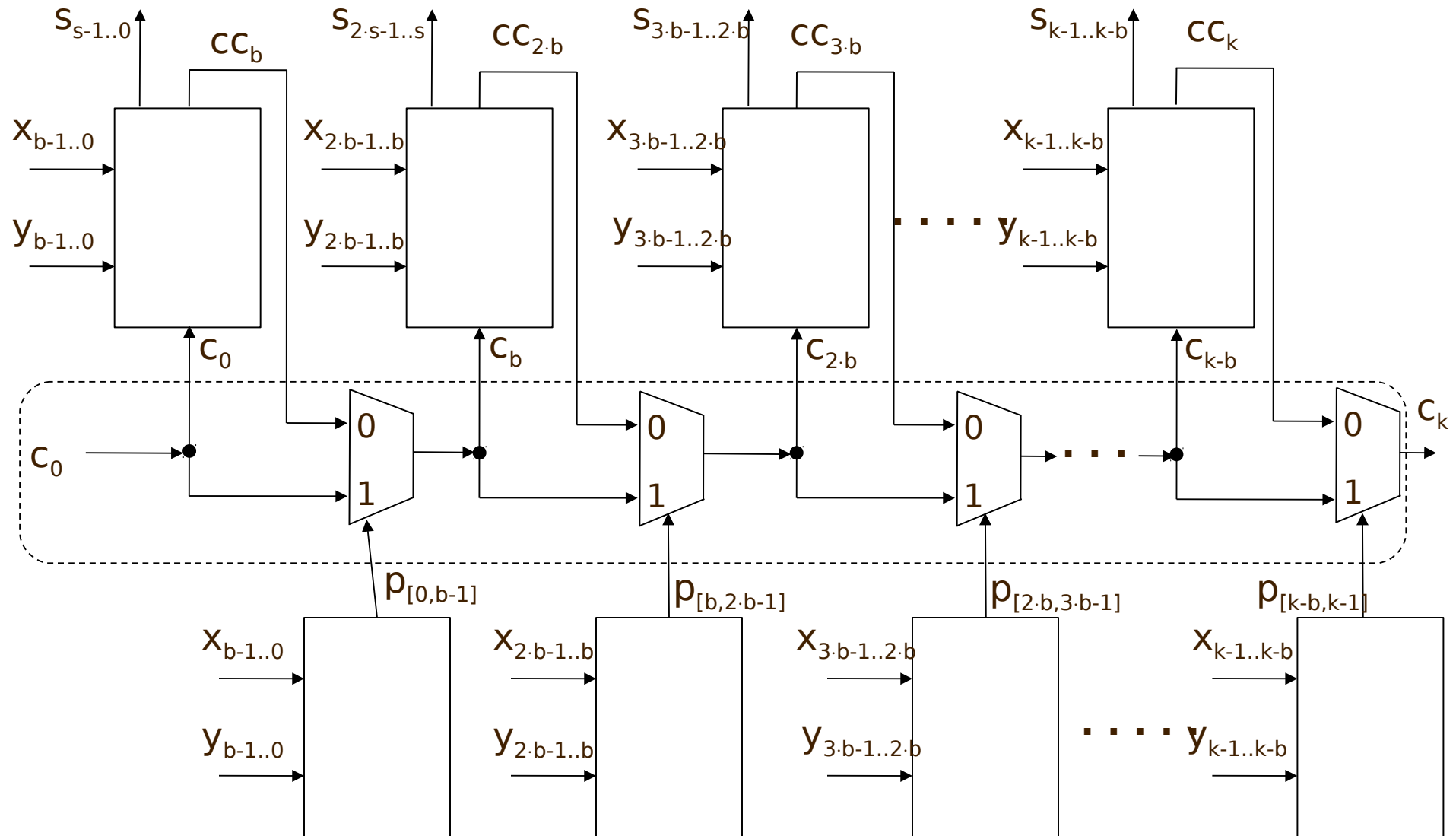

Carry-Skip Adders

in Xilinx Spartan II FPGAs

by J-P. Deschamps, G. Bioul, G. Sutter

k	Delay in ns				Max. Frequency
	b=k	b=8	b=16	b=32	Increase
14		13	12		13
16		14	13		21
23		14	14		63
38		-	16	17	141
77		-	20	20	29
159		-	28	25	53

Carry-Skip Adders

in Xilinx Spartan II FPGAs

by J-P. Deschamps, G. Bioul, G. Sutter

k	Area in CLB slices				Area Overhead		
	b=k	b=8	b=16	b=32	b=8	b=16	b=32
32		47	41	-	47%	28%	
48		73	66	-	52%	38%	
64		99	91	-	55%	42%	
128		-	191	179	-	49%	
256	-	391	375	-	53%	46%	
512		-	791	767	-	54%	

Carry-Skip Adders

Variable-Block-Size

Carry-Skip Adder with Variable-Width Blocks

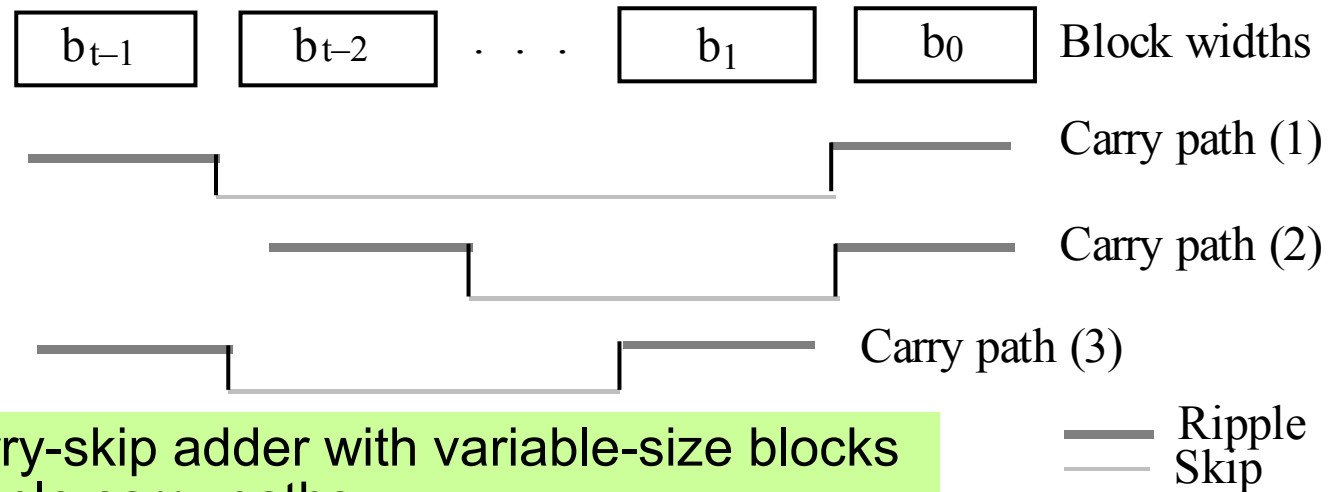


Fig. 7.2 Carry-skip adder with variable-size blocks and three sample carry paths.

The total number of bits in the t blocks is k :

$$2[b + (b + 1) + \dots + (b + t/2 - 1)] = t(b + t/4 - 1/2) = k$$


$$b = k/t - t/4 + 1/2$$

$$T_{\text{var-skip-add}} = 2(b - 1) + 0.5 + t - 2 = 2k/t + t/2 - 2.5$$


$$dT/db = -2k/t^2 + 1/2 = 0 \quad \Rightarrow \quad t^{\text{opt}} = 2\sqrt{k}$$

$$T^{\text{opt}} = 2\sqrt{k} - 2.5 \quad (\text{a factor of } \sqrt{2} \text{ smaller than for fixed-block})$$

Most critical path to produce carry

 

Most critical path to assimilate carry

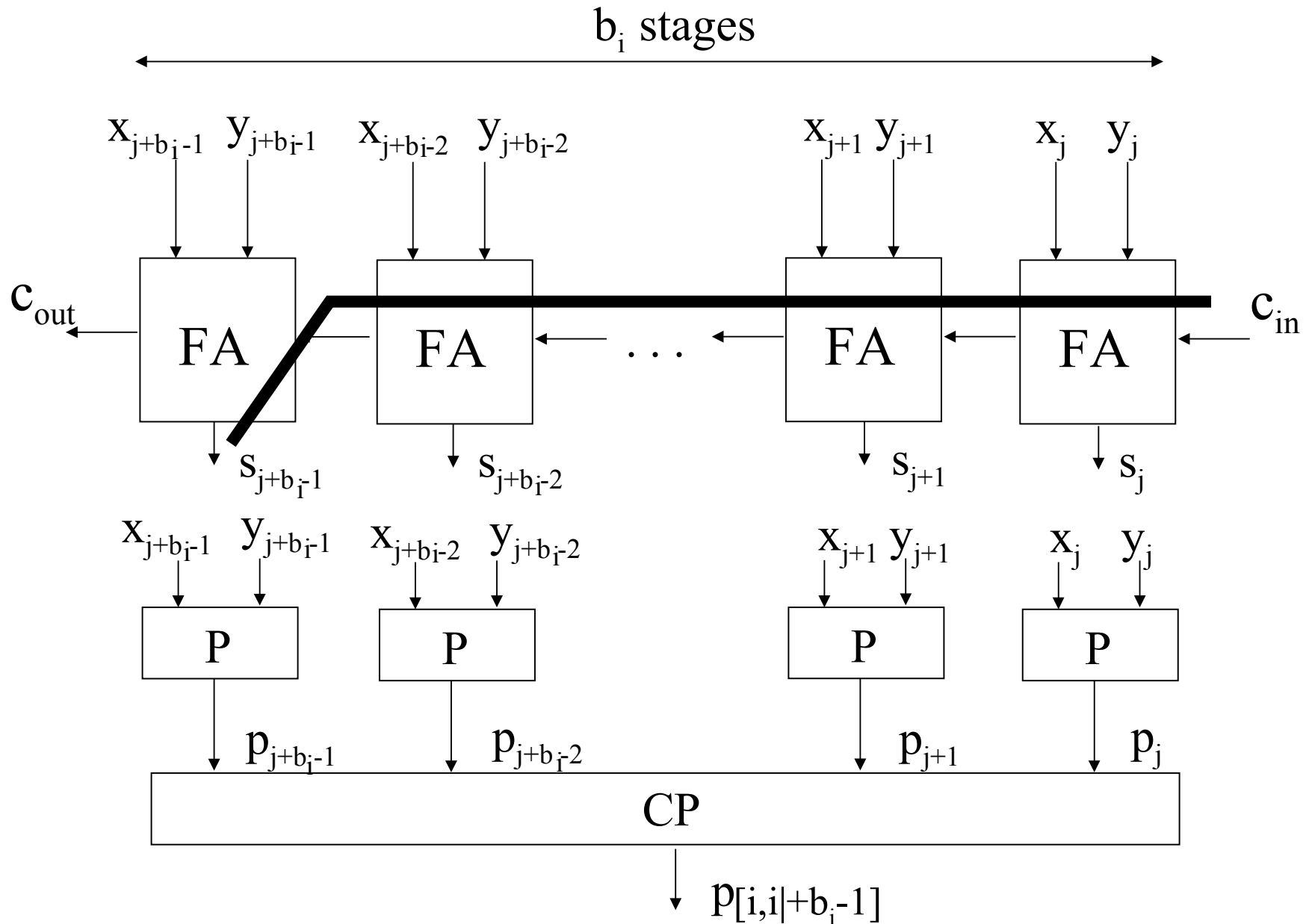

Variable-Block-Size Carry-Skip Adder (1)

Notation & Assumptions

Adder size - k -bits

Number of stages - t

Block size - variable

First and last block size - b bits

Delay of skip logic = Delay of one stage of ripple-carry adder
= 1 delay unit

Variable-Block-Size Carry-Skip Adder (2)

Optimum block sizes

$$\begin{array}{ccccccccccc} b_{t-1} & b_{t-2} & b_{t-3} & \dots & b_{t/2+1} & b_{t/2-1} & \dots & b_2 & b_1 & b_0 \\ b & b+1 & b+2 & \dots & b+\frac{t}{2}-1 & b+\frac{t}{2}-1 & & b+2 & b+1 & b \end{array}$$

Total number of bits

$$\begin{aligned} k &= 2 \left[b + (b+1) + (b+2) + \dots + \left(b + \frac{t}{2} + 1 \right) \right] = \\ &= t \left(b + \frac{t}{4} - \frac{1}{2} \right) \end{aligned}$$

Variable-Block-Size Carry-Skip Adder (3)

Number of bits in the first and last block

$$b = \frac{k}{t} - \frac{t}{4} + \frac{1}{2}$$


Latency of the carry-skip adder with variable block width

$$\begin{aligned}
 \text{Latency}_{\text{fixed-carry-skip}} &= \underbrace{(b - 1)}_{\text{in block 0}} + \underbrace{0.5}_{\text{OR gate}} + \underbrace{t - 2}_{\text{skips}} + \underbrace{(b - 1)}_{\text{in last block}} \\
 &= 2b + t - 3.5 = 2 \left[\frac{k}{t} - \frac{t}{4} + \frac{1}{2} \right] + t - 3.5 = \\
 &= \frac{2k}{t} + \frac{1}{2}t - 2.5
 \end{aligned}$$

Variable-Block-Size Carry-Skip Adder (4)

Optimal number of blocks

 
$$\frac{d\text{Latency}_{\text{variable-carry-skip}}}{dt} = -\frac{2k}{t^2} + \frac{1}{2} = 0$$



$$t_{\text{opt}} = \sqrt{4k} = 2\sqrt{k}$$

$$b_{\text{opt}} = \frac{k}{t_{\text{opt}}} - \frac{t_{\text{opt}}}{4} + \frac{1}{2} =$$
 
$$= \frac{k}{2\sqrt{k}} - \frac{2\sqrt{k}}{4} + \frac{1}{2} = \frac{1}{2}$$



$$b_{\text{opt}} = 1$$

Variable-Block-Size Carry-Skip Adder (5)

Optimal latency

$$\begin{aligned}\text{Latency}_{\text{variable-carry-skip}}^{\text{opt}} &= \frac{2k}{t} + \frac{1}{2} t - 2.5 = \\ &= \frac{2k}{2\sqrt{k}} + \frac{2\sqrt{k}}{2} - 2.5 = \\ &= 2\sqrt{k} - 2.5\end{aligned}$$

$$\text{Latency}_{\text{variable-carry-skip}}^{\text{opt}} \approx \frac{\text{Latency}_{\text{fixed-carry-skip}}^{\text{opt}}}{\sqrt{2}}$$